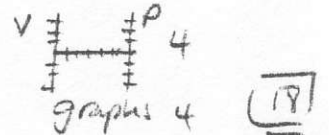


1. An a.c. supply, 6 V rms, 100 Hz, is connected to a 50 Ω resistor


- Calculate the peak voltage V_{peak} . (2)
- Explain what "r.m.s. voltage" means. (2)
- Calculate I_{rms} , and I_{peak} . (3)
- Calculate average power, P_{rms} , and peak power. (3)
- On the same axes, sketch graphs of ...
(i) Voltage vs. Time (ii) power vs. time



2. A student tests a wire coil...

- With 12 V d.c., steady current = 1.3 A. Coil resistance? (2)
- With 8 V rms, 500 Hz, $I_{rms} = 0.51$ A
Inductive reactance? (2)
- Coil self inductance? (2)
- Calculate peak values of p.d. across coil + current through it. (2)
- When an iron core is put in the coil, the current drops to 25 mA. Calculate the new self inductance and explain why the current is smaller. (4) (12)

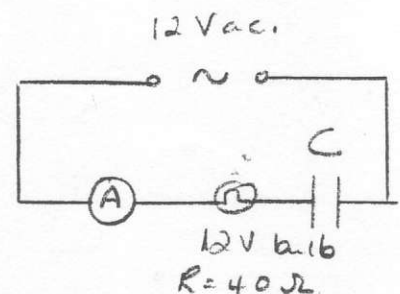3. A 12 V rms a.c. supply is connected to the circuit shown. At $f = 50$ Hz the rms current is 30 mA



- Calculate the capacitive reactance. (2)
- Calculate the capacitance. (2)
- As the frequency is increased, the bulb glows brighter, why? (3)
- Sketch a graph of current against frequency. (4) (11)

4. An LCR radio tuning circuit has an inductor of 800×10^{-9} H, and capacitor of 3.3×10^{-12} F. What is its resonant frequency? If you want to tune down to 87.5 MHz, what value of C do you need? (L is kept constant). (4)

- 1 a) $V_{rms} = V_{peak} / \sqrt{2}$ ⁽¹⁾ so $V_{peak} = 6 \times \sqrt{2} = 8.5 \text{ V}$ ⁽²⁾
 b) V_{rms} is the steady d.c. voltage ⁽¹⁾ that produces the same power. ⁽²⁾
 c) $I_{rms} = V_{rms} / R = 6 / 50 = 0.12 \text{ A}$ ⁽¹⁾
 $I_{peak} = V_{peak} / R = 8.5 / 50 = 0.17 \text{ A}$ or $I_{peak} = \sqrt{2} \times I_{rms} = 0.17 \text{ A}$ ⁽³⁾
 d) $P_{rms} = I_{rms} V_{rms} = 0.12 \times 6 = 0.72 \text{ W} = I_{rms}^2 R = 0.72 \text{ W}$ ⁽²⁾
 $P_{peak} = I_p V_p = I_p^2 R = 1.44 \text{ W}$ ⁽¹⁾ (note $P_{peak} = 2 \times P_{rms}$)

(e) for $f = 100 \text{ Hz}$

time period $T = 1/100 = 0.01 \text{ sec}$

3 axes labelled ⁽¹⁾


3 scales, V, I, Watts ⁽³⁾

V graph - shape ⁽¹⁾

- peak height ⁽¹⁾

Power - shape ⁽¹⁾

- peak height ⁽¹⁾

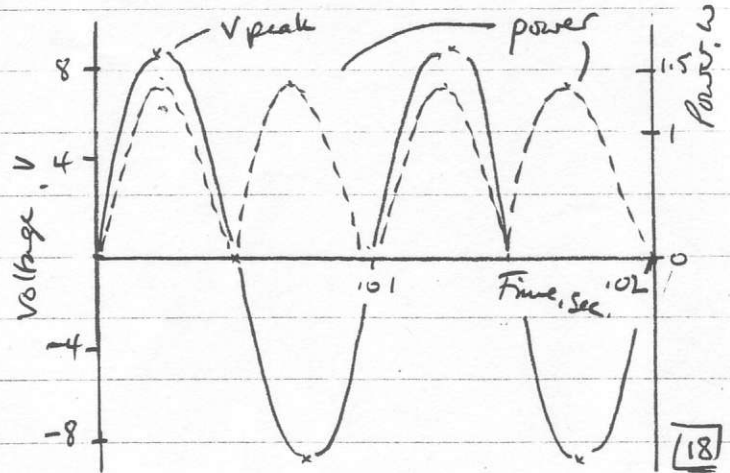

2 (a) D.C. ... $R = V/I = 12/1.3 = 9.23 \Omega$ ⁽¹⁾

(b) $X_L = V_{rms} / I_{rms} = 9 / 0.51 = 15.7 \Omega$ ⁽¹⁾

(c) $X_L = 2\pi f L \rightarrow L = X_L / 2\pi f = 15.7 / 2\pi 500 = 0.0049 \text{ Henries}$ ⁽¹⁾

(d) $V_{peak} = V_{rms} \times \sqrt{2} = 11.3 \text{ V}$ ⁽¹⁾ $I_{peak} = \sqrt{2} \times I_{rms} = 0.72 \text{ A}$ ⁽¹⁾

(e) Iron core ... new $X_L = 8 / 25 \times 10^{-3} = 320 \Omega$ ⁽¹⁾

so $L_{new} = X_L / 2\pi f = 320 / 2\pi 500 = 0.1 \text{ Henries}$ ⁽¹⁾

Smaller current because ... flux through coil is bigger, ⁽¹⁾

so faster change in flux, so induced back emf is larger ⁽²⁾

3. (a) $X_C = V_{rms} / I_{rms} = 12 / 30 \times 10^{-3} = 400 \Omega$ ⁽¹⁾

(b) $X_C = 1/2\pi f C \rightarrow C = 1/2\pi f X_C = 7.96 \times 10^{-6} \text{ F}$ ⁽¹⁾

(c) bulb brighter because ... C is

charged more times per second, ⁽¹⁾

so more charge passes through bulb ⁽¹⁾

per second so current larger ⁽¹⁾ (11)

(d) $I_{rms} = V_{rms} / X_C = V_{rms} \times 2\pi f C \dots I_{rms} \propto f$


4. $f_0 = 1/2\pi \sqrt{LC} = 1/2\pi (800 \times 10^{-9} \times 3.3 \times 10^{-12})^{1/2} = 97.9 \times 10^6 \text{ Hz}$ ⁽¹⁾

to find C for $f_0 = 87.5 \text{ MHz} \dots$

rearrange $f_0^2 = 1/4\pi^2 LC \rightarrow C = 1/4\pi^2 L f_0^2 = 4.1 \times 10^{-12} \text{ F}$ ⁽¹⁾

(to reduce freq you need a bigger C.)

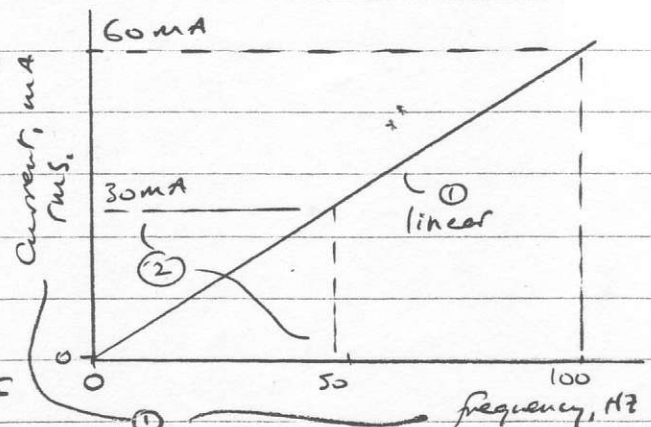Q ... $1/18 \quad 2/12 \quad 3/11 \quad 4/4$



Radio 1!

(4)