


Capacitors - Questions. ①

A Physics
Capacitor

1. (a) What is the definition and unit of Capacitance? (2) $e = -1.6 \times 10^{-19} \text{ C}$
- (b) A $2200 \mu\text{F}$ capacitor is connected to a 1.5 V cell. What charge is stored? How many electrons is this? Draw the circuit and show where the electrons are. (5)
- (c) How much energy is stored in the capacitor? (2)
- (d) If you wanted to store 0.1 J energy at the same p.d., what capacitance would you need? (2) [9]

2. (a) You have three $12 \mu\text{F}$ capacitors. Draw the 4 ways of combining them and calculate the total capacitance of each. (8)
- (b) If each capacitor can withstand 10 V , how can you arrange them to have a total capacitance of $8 \mu\text{F}$, that can withstand 30 V ? (You will need more than 3 capacitors, but less than 10!) (2) [10]

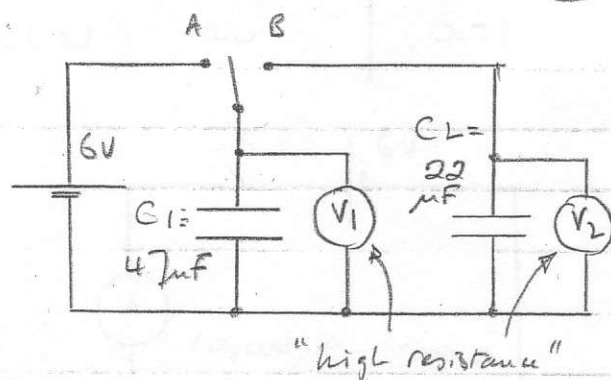3. In the circuit shown, the switch is moved to A for a short time, then moved to B.



- (a) What is the reading on V_1 , with switch at A? (2)
- (b) When the switch is moved to B, what happens to the charge, and the p.d. across each capacitor? (3)
- (c) What are the new readings on each voltmeter? (4)
- (d) What is the total energy delivered by the battery to charge C_1 ? (2)
- (e) What is the energy stored by C_1 at 6 V ? (2)
- (f) What is the energy stored by C_1 and C_2 together, with the switch at B? (2)
- (g) Can you explain the differences between answers (e), (f) and (g)? (2) [17]

Capacitors — Questions — ②

A Physics


4. An $8.0 \mu\text{F}$ capacitor is charged to 50V
 A $4 \mu\text{F}$ capacitor is charged to 200V .
- Calculate the charge and energy stored in each. (2×3)
 - They are then joined in parallel.
 Calculate the new p.d. across each, the charge stored in each, and the energy stored by each. (3×2)
 - Draw a diagram to show where the charge flows when they are connected. (2)
 - Explain the change in energy stored. (2) 16

5. A capacitor is discharged through a $12 \text{ k}\Omega$ resistor, and the capacitor p.d. falls as shown →

time (Sec.)	p.d. (volts)
0	9.6
20	5.8
40	3.5
60	2.1
80	1.3
100	0.77

- Plot the p.d./time graph. (4)
- Estimate the "half life" — the time for p.d. to halve. (2) 18
- Calculate the value of capacitance. (2)

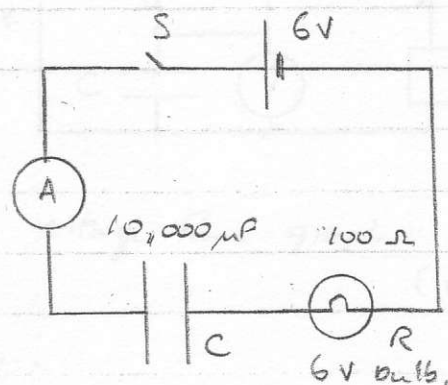6. With C initially uncharged, switch S is closed.




- What is the initial current in the circuit? (2)
- What is the final p.d. across C? (1)
- What is the time constant? (2)
- What is the "half life" time $t_{1/2}$? (2)
- Sketch graphs of voltage across C, and current through bulb against time. (2×4)
- Describe and explain what happens in the circuit as C charges up. (3) 18

Capacitors - Questions - ③


A Physics

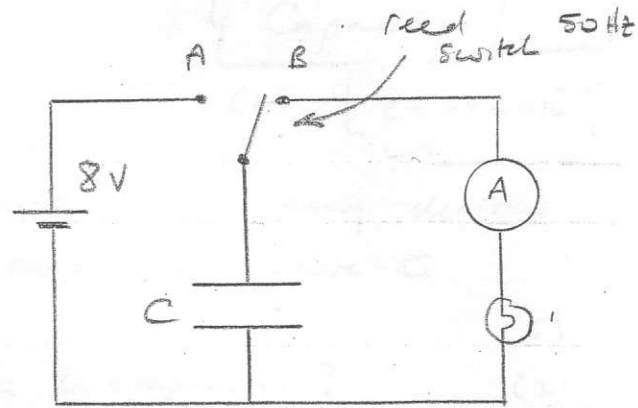7. The reed switch operates at 50 Hz to charge C from the battery, and discharge it through the bulb. The ammeter shows a current of 32 mA flows



- What is the charge flowing each second? (1)
- Calculate the value of C . (2)
- Sketch a graph to show how the capacitor p.d. varies over 1 cycle of charge and discharge. (5)
- Will the capacitor be fully charged in the time available? Explain your answer. (3) 11

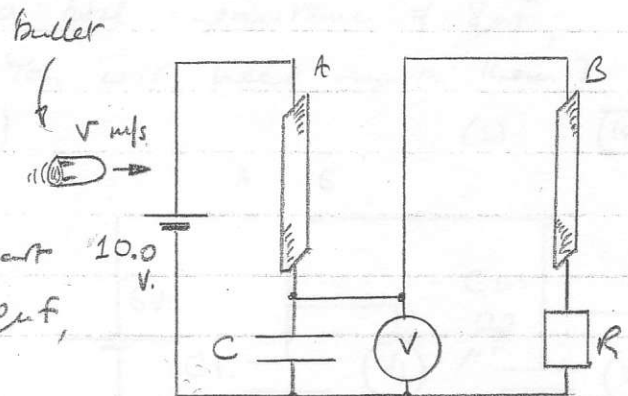8. This arrangement is used to measure the speed of a bullet. A and B are thin strips of aluminium foil, 0.2 m apart. The cell has a p.d. of 10.0 V, $C = 2.0 \mu\text{F}$, and $R = 800 \Omega$.



- Calculate CR , and $t_{1/2}$. (2)
- Use these figures to plot (not sketch) the voltage time graph. (for times up to $3 \times t_{1/2}$). (4)
- Data from measurement of bullet speed...
p.d. before bullet is fired. - 10.0 V.
p.d. after bullet has broken strips A and B - 4.1 V
Use your graph to find the time delay between A and B. (2)
- What is the speed of the bullet? (2)
- Explain briefly how this arrangement is used to measure the speed of a bullet. (4) 14

Capacitors - Answers - Q 1-4


A Phys. in Capacitors

1. (a) charge stored / volt of p.d. Find (2)





(b) $Q = CV = 3.3 \times 10^{-3} \text{ C} = 2.1 \times 10^{16} \text{ electrons}$ / 5

(c) Energy = $\frac{1}{2} QV = \frac{1}{2} CV^2 = 2.5 \times 10^{-3} \text{ J}$ / 2

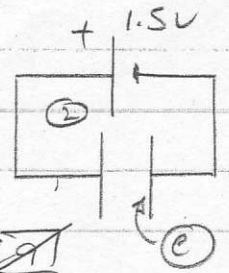(d) $C = 2 \times \text{energy} / V^2 = 2 \times 0.1 / 1.5^2 = 0.089 \text{ Farad}$




2. (a)

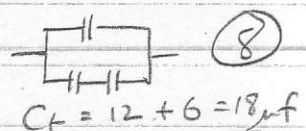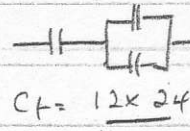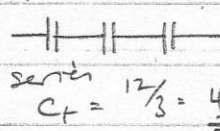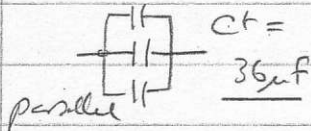

(b) You need 3 Caps in series $\rightarrow$ $C_T = 4 \mu\text{F}$ $V_{\text{max}} = 20\text{V}$

so you need ...

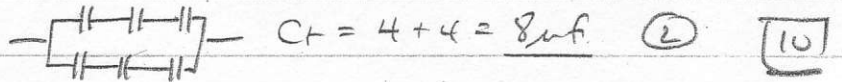

3. (a) $V_1 = 6\text{V}$ (2)

(b) Charge flows $C_1 \rightarrow C_2$ until p.d.s equal (1) / 3

(c) use $Q = CV$ Q constant at $Q = CV = 47 \times 10^{-6} \times 6 = 2.82 \times 10^{-4} \text{ C}$ (2)

New $C_T = 47 + 22 = 69 \mu\text{F}$ (1)

so p.d. across both $V = Q / C_T = 2.82 \times 10^{-4} / 69 \times 10^{-6} = 4.1 \text{ V}$ / 4

(d) energy from battery $E_{\text{batt}} = Q \times V_{\text{batt}} = 2.8 \times 10^{-4} \times 6 = 1.69 \times 10^{-3} \text{ J}$ (2)

(e) E stored by C_1 , $E_{C1} = \frac{1}{2} CV^2 = 8.5 \times 10^{-4} \text{ J}$ (2)

(f) E on $C_1 + C_2$, $E_{\text{final}} = \frac{1}{2} C_T V^2 = \frac{1}{2} Q V_{\text{final}} = 5.8 \times 10^{-4} \text{ J}$ (2)

(g) Each time charge flows, energy is lost in overcoming resistance of wires and heating them up.


Energy lost (1) flow of charge battery $\rightarrow C_1$ (2) charge flow $C_1 \rightarrow C_2$ (2) (17)

4. (a) $\frac{50\text{V}}{8\mu\text{F}} \rightarrow E = \frac{1}{2} CV^2 = 0.01 \text{ J}$ $\frac{4\mu\text{F}}{200\text{V}} \rightarrow E = \frac{1}{2} CV^2 = 0.08 \text{ J}$ (6)

$Q = CV = 4 \times 10^{-4} \text{ C}$ (3)

$Q = CV = 8 \times 10^{-4} \text{ C}$ (3)

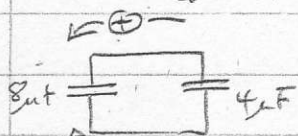(b) $Q_T = 12 \times 10^{-4} \text{ C}$ so new p.d $V = \frac{Q_T}{C_T} = 100 \text{ V}$



$Q_{8\mu\text{F}} = CV = 8 \times 10^{-6} \times 100 = 8 \times 10^{-4} \text{ C}$

$Q_{4\mu\text{F}} = CV = 4 \times 10^{-4} \text{ C}$

$E_{8\mu\text{F}} = \frac{1}{2} QV = 4 \times 10^{-2} \text{ J}$

$E_{4\mu\text{F}} = \frac{1}{2} QV = 2 \times 10^{-2} \text{ J}$ $E_T = 6 \times 10^{-2} \text{ J}$

(c) charge flows $4\mu\text{F} \rightarrow 8\mu\text{F}$

(d) Initially $E_T = 0.09 \text{ J}$ } lost as heat when
Finally $E_T = 0.06 \text{ J}$ } charge flows in wires

TW 3.98 (phys!)

Capacitors - Q 5-8 ~~Answers~~ 1/2

A Physics


5. (a) graph... 1/4

(b) $t_{1/2} = 27 \text{ s}$ 1/2

(c) $t_{1/2} = 0.69 CR$

$\rightarrow C = 3.3 \times 10^{-3} \text{ F}$

(8)

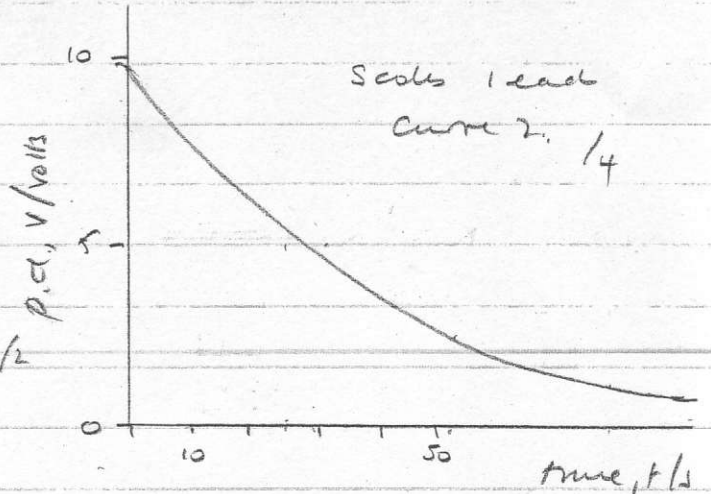

6. (a) $I_0 = V_0/R = 6/100 = 0.06 \text{ A}$

(b) $V_{\text{final}} = 6 \text{ V.!!}$ 1/1


(c) $EL = 1 \text{ sec}$ 1/2

(d) $t_{1/2} = 0.69 CR = 0.69 \text{ s}$ 1/2

(e) graphs... labels (1), scales (2), plot (1)

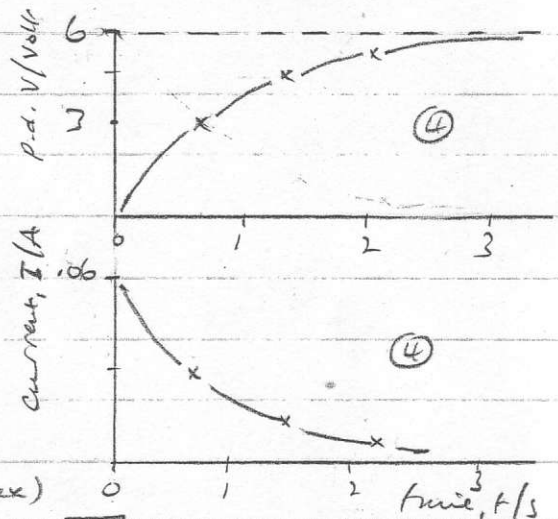(f) as C charges up...

Electrons flow ⁽¹⁾ and current (clockwise), large initial current, as p.d. builds up ⁽¹⁾ across C, opposing cell p.d., current falls ⁽¹⁾ exponentially, approaching zero




(3 max)

7. (a) charge/sec, $Q = I = 32 \times 10^{-3} \text{ A} = \text{C/s}$ 1/1 (18)

(b) Current = $Q/\text{sec} = CVf \rightarrow C = I/Vf = 32 \times 10^{-3} / 8 \times 50 = 80 \mu\text{F}$ 1/2

(c)

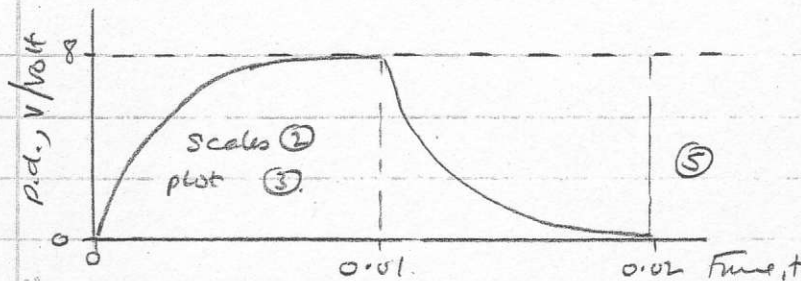

You need R-value for this!
 $t_{1/2} = 0.69 CR$ should be
 $\ll 0.01 \text{ sec}$ for C to fully
 charge/discharge. 1/3.

8. (a) $CR = 1.6 \times 10^{-3} \text{ s}$ $t_{1/2} = 1.1 \times 10^{-3} \text{ s}$ 1/2


(b) from graph... t delay should be $1.43 \times 10^{-3} \text{ sec}$ (2)

(c) $V = d/t = 0.2 / 1.43 \times 10^{-3} = 140 \text{ m/s}$ (12)

(d) Bullet breaks strip A, C starts discharging as bullet travels to B.

Bullet breaks B, stops C discharging.

Time for travel A-B found from V drop.

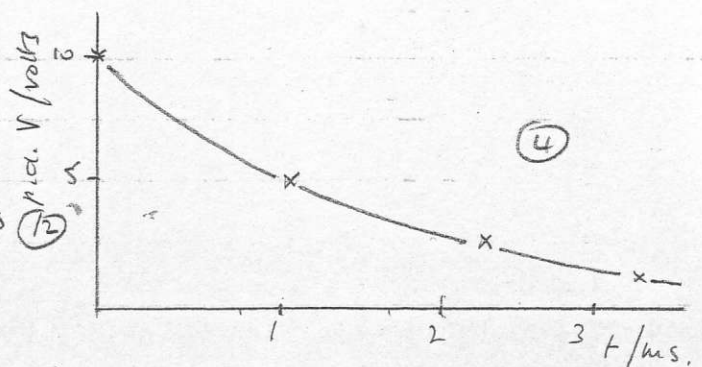

SW
3.98

(14)