

Capacitors - Topic Test

A level Physics 1

1. Explain fully the meaning, with definitions, of...

(a) Capacitance (3)

(b) Time constant (3)


[6]

2. In the circuit shown $\rightarrow$
switch S is closed, with C uncharged.
What are ...

(a) initial and final current values? (3)

(b) initial and final voltmeter readings? (2)

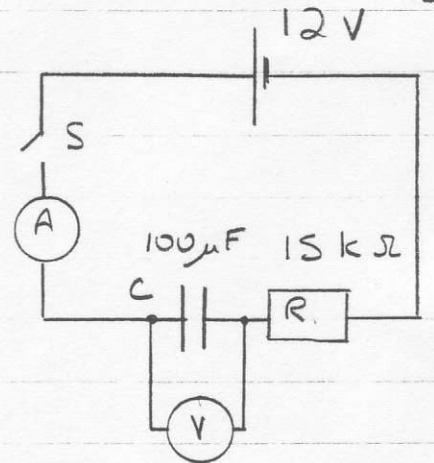(c) What is the time constant of the circuit? (2)




Sketch graphs to show how...

(d) current changes with time (4)

(e) voltage across C changes with time (4)

(f) What does the area under the I/t curve show? (1) [16]

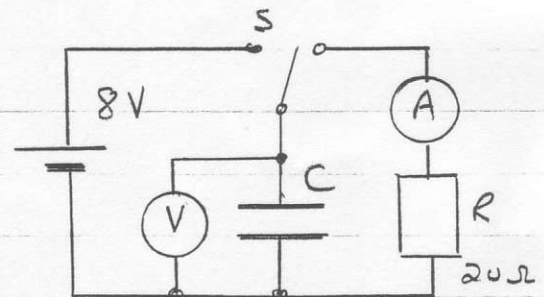3. The reed switch S operates at 250 Hz. The ammeter shows a current of 120 mA is flowing through it.



(a) What is the value of C ? (3)

(b) The student doubles the resistance, and notices the current falls. Explain why this happens. (2) [5]


4. The switch is moved to A.

(a) Calculate the charge and energy stored in C_1 (4)

The switch is moved to B.

(b) Calculate the charge and energy stored in C_1 and C_2 together. (3)

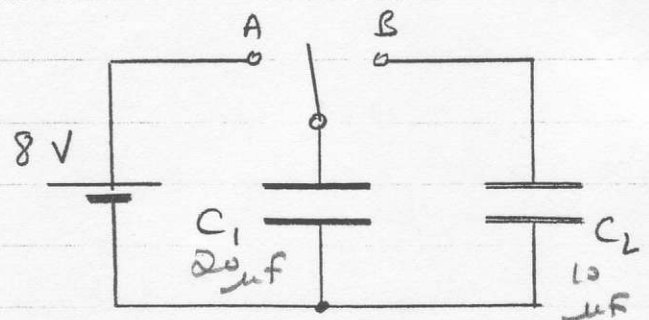(c) Explain the difference in energy values. (2) [9]




5. How can you combine " $1 \mu F$, 10V" capacitors, to give

you a $1 \mu F$ capacitance, that can withstand 20V? (2)

Capacitors


ANSWERS

A-level Physics

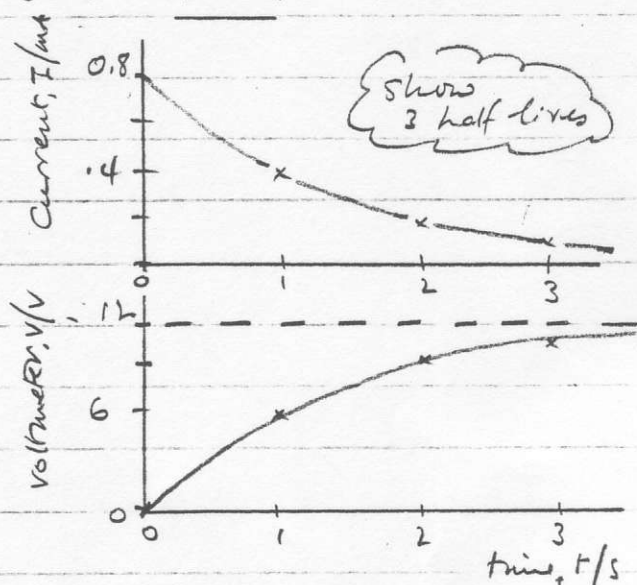- 30 1 (a) Capacitance - charge (C) stored per volt $C = Q/V$ Farad = Coulombs/volt $\frac{1}{3}$
- (b) Time constant $= C \times R$ (sec) Farad Ohm $t_{1/2} = 0.69 CR$ $\frac{1}{3}$
2. (a) $I_{initial} = V/R = 12/15000 = 8 \times 10^{-4} A$ $I_{final} = 0$!! (3) 6
- (b) $V_{initial} = 0 V$ $V_{final} = 12 V$!! (2)
- (c) time constant $= CR = 100 \times 10^{-6} \times 15 \times 10^3 = 1.5 s$ (2)
- So $t_{1/2} =$ time for $\left\{ \begin{matrix} \text{current} \\ \text{voltage} \end{matrix} \right\}$ to halve
 $= 0.69 CR = 1.04 s$
- (d) Current: I falls exponentially. (4)
- (e) Voltage: rises towards 12V (4)
- marking axes - labelled & scales $\frac{1}{2}$ each
 curve - (2)
- (f) Area under $I/t =$ charge stored 16
- 

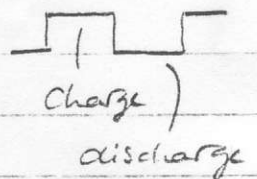3. (a) Charge/sec $Q = I \times t = CVf = 120 mA$
 so $C = 0.12/8 \times 250 = 60 \times 10^{-6} F = 60 \mu F$ (3)
- (b) Time constant $CR = 60 \times 10^{-6} \times 200 = 1.2 ms$

at 250 Hz time for discharging is $\frac{1}{2}$ of $\frac{1}{250} s$.
 which = 2 ms. C just has time to discharge fully
 before being recharged. If you double R, T.C. will
 double, and C will not fully discharge. (2)



(It's not following Ohm's Law $I = V/R$!)


4. (a) switch at A $Q = CV = 20 \times 10^{-6} \times 8 = 1.6 \times 10^{-4} C$
 energy $E = \frac{1}{2} CV^2 = \frac{1}{2} \times 20 \times 10^{-6} \times 8^2 = 6.4 \times 10^{-4} J$

- (b) switch to B total charge stays constant $\frac{1}{2}$

$C_{total} = 30 \mu F$ $E = \frac{1}{2} QV = \frac{1}{2} CV^2 = \frac{1}{2} \frac{Q^2}{C} = 4.3 \times 10^{-4} \text{ Joules}$
 (you don't really need to calculate new p.d. ... $\frac{2}{3}$ of 8)
 but if you did it would be $V_{new} = Q/C_{new} = \frac{1.6 \times 10^{-4}}{30 \times 10^{-6}} = 5.3 V$

- (c) Energy lost as heat in wires as charge moves/current flows. (2) 9

5.  $= 0.5 \mu F$ max 20V

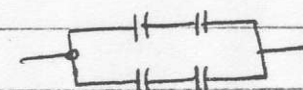So...  $= 1 \mu F$ max 20V. (2)

Total/38