

Electromagnetic Induction

Topic
Test

A Physics

* 5(a)
cell
p.d.

1. Define with suitable words, formulas, units,...

(a) Faraday's Law - basic Law, and formulas for (i) wire cutting flux (ii) flux changing in a coil (5)

(b) Lenz's Law. (2)

7

A retired Physics Teacher gets a job as a Lighthouse keeper, and builds his own alternator + power supply.


2. The Alternator

Basic data: flux density 0.8 T , coil size $6 \text{ cm} \times 10 \text{ cm}$

(a) Which way will electrons flow in AB when the coil is rotated as shown? (1)

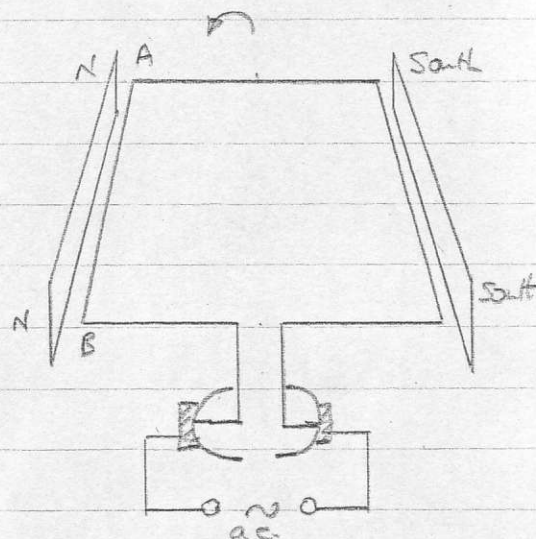(b) The alternator must produce a.c. with a peak voltage of 380 V , and frequency of 50 Hz .

How many turns of wire should be on the rotating coil? (2)



(c) Sketch a graph (labelled axes + scales) to show 2 complete cycles of the output (5)

(d) Mark on the graph ...

H - where the coil is horizontal (parallel to field)

V - where coil is vertical (at 90° to field) (2)


10

3. The Transformer

The alternator supplies a.c.

at a p.d. of 260 V , and a current of 800 mA

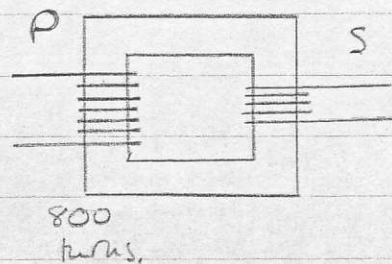A 12 V supply is needed to run the radio,



(a) How many turns should be on the secondary coil? (2)

©

TW

12.98

Summary ...

1

7

2

10

3

10

4

7

5

22

Total

57

Inductance - Test / 2

A Physics



- 3 (b) If the transformer is 85% efficient, what is the maximum current it can deliver at 12V? (3)
- (c) In what form is the energy lost? (1)
- (d) What are the 4 ways that the transformer loses energy? (4)

10

4. The Rectifier

Alternator

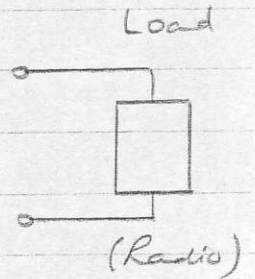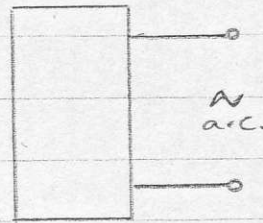- (a) The lighthouse keeper wants a smooth d.c. supply. Copy the diagram and add to it to show how this can be done (4)




- (b) Sketch and label a simple current/time graph (no scales) to show (i) half wave rectified d.c. (ii) the smoothed waveform. (3)

7

The Inductor

5. The diagram shows a pure inductor in series with a resistor

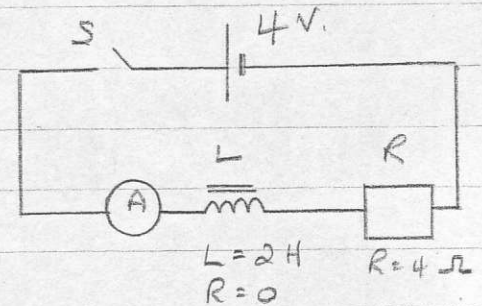- (a) "The inductor has a self-inductance of 2 H" - what does this mean? (2)



- (b) At the moment the current is switched on, what is ...

- current in circuit? (1)

- p.d. across L? (2)

- p.d. across R? (1)

- (c) Calculate ...

- the final current. (2)

- the initial rate of current rise (2)

- (d) Sketch a graph (axes + scales) to show how current changes with time from switching on. (4)


- (e) Explain the shape of the graph. - at short and long times (4 + 2)

- (f) Explain the effect of (i) decreasing L only (1)
(ii) decreasing R only (1)

22

2.99
2.99
2.99

E.M. Induction - Test

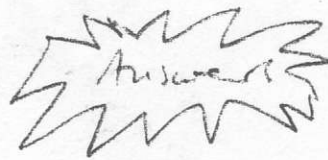

A Physics

1. (a) E.M.F induced is proportional to the rate of flux linkage cutting or the rate of change of flux linkage through the circuit ①

Wire cutting flux

$$E = B l v$$

emf volts / (flux density in Velocity m/s)

Flux in coil

$$E = N \frac{d\Phi}{dt}$$

emf turns / (change in flux/sec T/sec)

- (b) Lenz - the direction of induced emf/current is always opposing the change that produced it

2. (a) R.H. Rule ... $A \rightarrow B$ ①

$$E_{max} = BAN 2\pi f$$

(c)

$$T = 1/f$$


$$= 0.02 \text{ sec}$$

$$\text{So } N = \frac{E_{max}}{BA 2\pi f} = 252 \text{ turns}$$

(2)

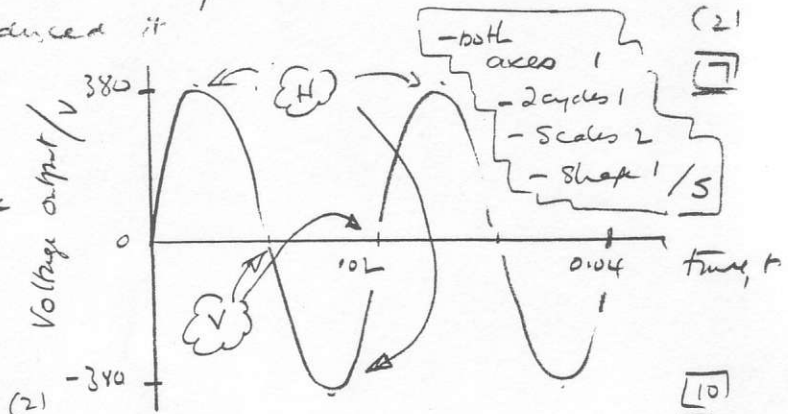- (d) H - max. rate of flux change $\rightarrow E_{max}$

$$V = 0 \text{ rate of flux change} \rightarrow E = 0$$



3. (a) $N_s/N_p = V_s/V_p \rightarrow N_s = \frac{12}{260} \times 800 = 37 \text{ turns}$

(2)

$$(b) I_p V_p = I_s V_s \rightarrow I_s = \frac{I_p V_p}{V_s} = \frac{0.8 \times 260}{12} = 17.3 \text{ A}$$

(3)

$$85\% \text{ efficiency} \rightarrow I_{at \text{ max}} = 17.3 \times 0.85 = 14.7 \text{ A}$$



- (c) Heat ①

heat in wire coils due to current

- (d) Copper losses - heat due to eddy currents

Iron losses - flux escaping from core energy needed to keep reversing flux in core

4. (a)

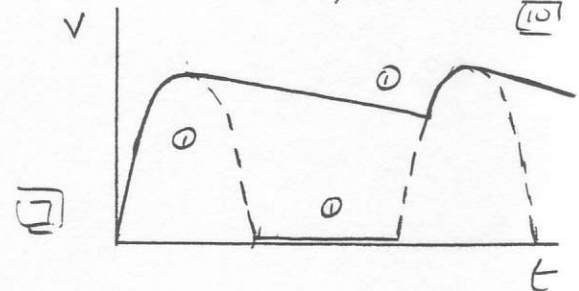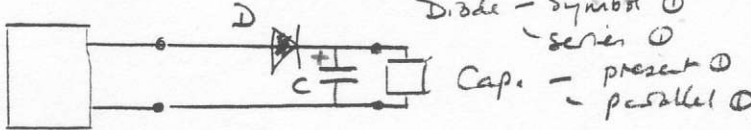

5. Sorry - answer missing.