

# Internal Resistance


1 of 2

AS Physics
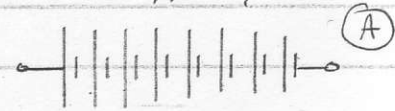
## 1. Starting your car.

need a current of 50 A or more

Car starter motors operate from nominally "12V" supplies, and A Physics student needs a new car battery (cost £24.99 at cheepo-mart.) and thinks "I can use 8 Zinc cells, and buy some Physics text books..."



8 Zinc cells  
each:  $E = 1.5 \text{ V}$ ,  $r = 0.4 \Omega$

a) What is the total e.m.f., and total internal resistance of 8 Zinc cells in series? (2)



b) How much current would these cells deliver if short circuited ( $R_{\text{ext}} = 0 \Omega$ )? (2)

6 lead cells  
each:  $E = 2.0 \text{ V}$ ,  $r = ? \Omega$

c) What would be the terminal voltage across the 8 cells? (2)

d) Would the zinc cells start the car? Explain your answer. (2)

e) The student buys a new car battery, and investigates.

She measures that while starting the engine...

battery p.d. = 10.8 V and current through motor = 60 A.

Calculate the resistance of the motor (3)

f) Calculate the total internal resistance of the battery. (3)

g) If the motor needs a minimum of 50 A to start the engine, what is the maximum internal resistance the battery can have? (3)

Q ... [1]

[2]

/17

/14

T2N

12.00

+ 11.04


# Internal Resistance

2 of 2

AS Physics
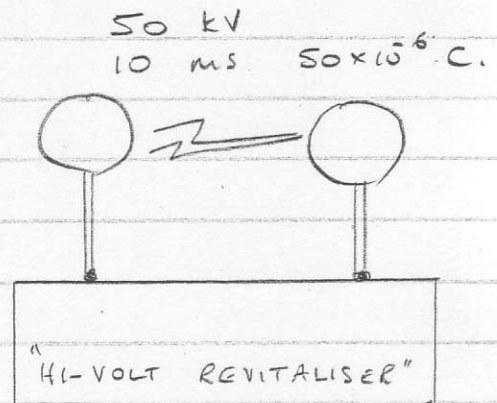
## 1. The Spark of Life

Baron Frankenstein is building his mark IV spark vitaliser. It delivers a spark at 50 kV lasting 10 milliseconds (10 ms).



a) What are the voltage and time duration of the spark in Volts? (2)

b) Calculate the current flowing in the spark (2)


c) How many electrons is this? (1)

electron charge  
 $e = -1.6 \times 10^{-19} \text{ C}$

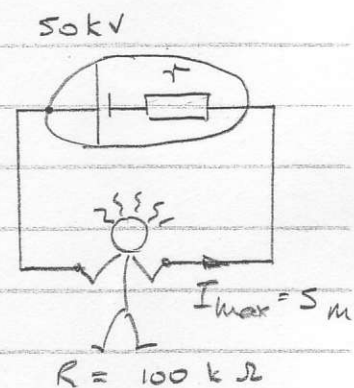d) The Baron is concerned for the safety of his assistant Igor, in case he touches the terminals.

He knows that body resistance is about  $100 \text{ k}\Omega$ , and the maximum safe current is  $5 \text{ mA}$ .

What internal resistance  $r$  should the Baron put in his machine to limit the current to  $5 \text{ mA}$ ? (3)



e) The Baron has two resistors; one of  $3.3 \text{ M}\Omega$  ( $3.3 \times 10^6 \Omega$ ) and the other of  $8.2 \text{ M}\Omega$ .

What is their combined resistance ... in series?

... in parallel? (2)

f) What is the current through Igor with the resistors and ... in series? (2)

... in parallel? (2)

Q.. [1]

17

[2]

14

T2N

+ 11.04

12.00

# Internal Resistance ~~Answers~~

AS Physics

1.  (a)  $E_{\text{total}} = 8 \times 1.5 = 12 \text{ V}$  and  $r_{\text{total}} = 8 \times 0.4 = 3.2 \Omega$

b) short circuit  $R_{\text{ext}} = 0 \Omega$  so  $E = IR + Ir$   
 $12 = 0 + I \times 3.2 \rightarrow I = 3.75 \text{ A}$


c) Since  $R = 0 \dots IR = 0 \dots V_{\text{terminal}} = 0 \text{ V} !!$

d) Nope ... current too small ... (limited by internal resistance)

e) look at the motor ... p.d. to motor  $= 10.8 \text{ V}$   $I = 60 \text{ A}$   
 so  $R_{\text{motor}} = V/I = 10.8/60 = 0.18 \Omega$

f) use  $E = IR + Ir$   $\rightarrow 12 = 10.8 + 60r$   
 so ...  $r_{\text{int}} = (12 - 10.8)/60 = 0.02 \Omega$

g) use  $E = IR + Ir = I(R + r)$   
 so  $12 = 50(0.18 + r_{\text{max}}) \rightarrow 12/50 = 0.24 = 0.18 + r_{\text{max}}$   
 $\rightarrow r_{\text{max}} = 0.24 - 0.18 = 0.06 \Omega$   
 or ...  $12 = (50 \times 0.18) + 50 \times r \rightarrow 12 - 9 = 3 = 50r \rightarrow r_{\text{max}} = 0.06 \Omega$


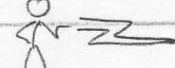
2.  (a)  $50000 \text{ V}$  and  $10/1000 = 10 \times 10^{-3} \text{ s}$

b)  $I = Q/t = 50 \times 10^{-6} / 10 \times 10^{-3} = 0.005 \text{ A}$  (5 mA)

c) no. electrons  $= 50 \times 10^{-6} / 1.6 \times 10^{-19} = 3.1 \times 10^{14}$

d) use  $E = IR + Ir$   $\rightarrow 50000 = 0.005 \times 100000 + 0.005 \times r_{\text{int}}$   
 $I_{\text{gav}} \nearrow$

so ...  $50000 = 500 + 0.005r \rightarrow r = 49500/0.005$   
 $= 9900000 \Omega$  (9.9 M)

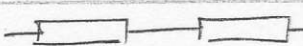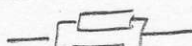e) series   $R_{\text{c}} = 11.5 \text{ M}\Omega$   
 parallel   $R_{\text{t}} = \frac{3.3 \times 8.2}{3.3 + 8.2} = 2.35 \text{ M}\Omega = 2.35 \times 10^6 \Omega$

f) series ...  $E = IR + Ir = I(R + r)$  use the exp key!  
 $50 \times 10^3 = I(100 \times 10^3 + 11.5 \times 10^6)$   
 so  $I = 50 \times 10^3 / 11.6 \times 10^6 = 0.0043 \text{ A}$  (4.3 mA)

parallel ...  $E = IR + Ir$   
 $50 \times 10^3 = I(100 \times 10^3 + 2.35 \times 10^6)$   
 so  $I = 50 \times 10^3 / 2.45 \times 10^6 = 0.020 \text{ A}$  (20 mA)

Y24  
12.00

Q 11 / 17

Q 12 / 14

Sony Igor!!  oops.