

Potential Dividers

1/2

Ats Phy 1.21


1. (a) State and explain what happens to the LDR resistance when it is illuminated (3)

(b) State and explain what happens to V_{out} when the LDR is illuminated (3)

(c) Calculate the value of V_{out} ...

(i) in the dark


(ii) in the light (3)

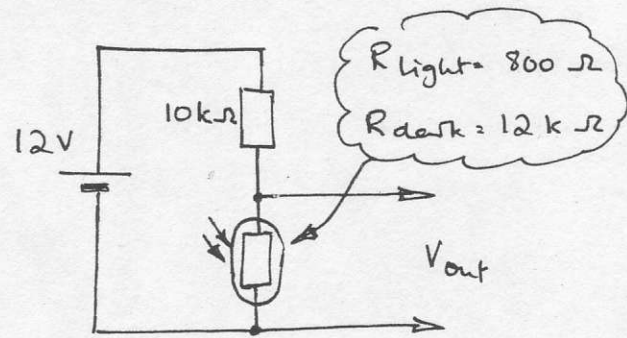

2. (a) Explain what x is and what it does in the circuit (2)

(b) What is the range of values of V_{out} that can be produced? (3)

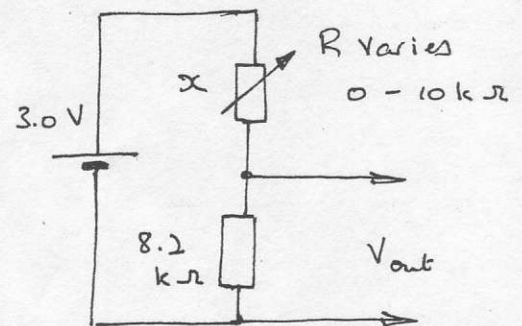(c) If $V_{out} = 1.5V$, what is the resistance of x ? (1)



3. This potential divider circuit acts as a temperature sensor.

(a) Explain how it works (5)

(b) Calculate the values of V_{out} ...


(i) cold

(ii) hot (3)

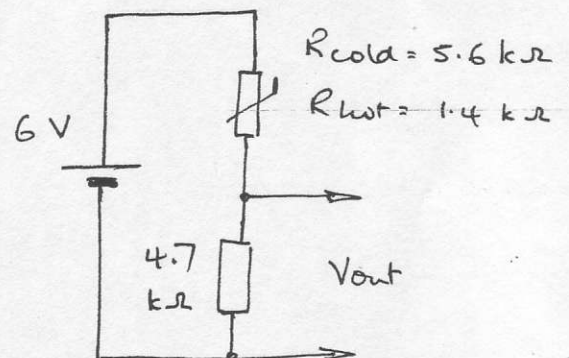(c) You want to be able to adjust

V_{out} to be 2.5V when the

thermistor is hot. Explain how to modify the circuit to do this. (3)



4. This is an electronic Scales


AB is a resistance coil, 5cm from A to B, with a total resistance of 10kΩ.

Sliding contact C can move up + down.

Contact C is fixed to platform P,

which hangs from spring S, which

has a spring constant of 250 N m⁻¹.

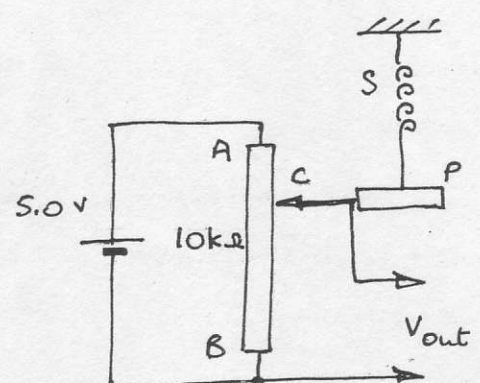

Q.4 continued

When there is no load on platform P, contact C is at A.

(a) Calculate V_{out} with....

(i) No load on platform P (1)

(ii) A weight of 4.0 N on P. (4)

(b) Sketch a graph to show how V_{out} depends on the weight on platform P, up to the maximum weight the device can measure (5)

(c) By using your graph, or otherwise, state what weight is on platform P when $V_{out} = 1.5$ V. (2)

Potential Divider

ANSWERS

AS Phys.:

1. (a) Light energy makes the atoms in the semiconductor Ldr vibrate with a bigger amplitude... this releases more electrons able to move + carry current... so $R \downarrow$



- b) R_{Ldr} decreases... so it has a smaller share of the total resistance... so V_{out} decreases.

c) i) dark $V_{out} = 12 \times \frac{12}{10+12} = 6.5 \text{ V}$ (you can work in $k\Omega$)

ii) light $V_{out} = 12 \times \frac{800}{10000+800} = 0.89 \text{ V}$ (be careful!)

2. (a) X is a variable resistor... used to adjust V_{out} to certain value

b) for $R_x = 0 \Omega$ $V_{out} = 3 \times \frac{8.2}{(8.2+0)} = 3.0 \text{ V}$ 2 s.f.

for $R_x = 10 k\Omega$ $V_{out} = 3.0 \times \frac{8.2}{8.2+10} = 1.4 \text{ V}$ 2 s.f.

- (c) Think! $V_{out} = \frac{1}{2}$ of V_{in} ... so $R_x = 8.2 k\Omega$!!

3. (a) when it gets hotter... atoms in thermistor vibrate with bigger amplitude... this releases electrons to move + carry current... so $R_{thermistor}$ decreases... so it has a smaller share of the total resistance... so it takes a smaller share of V_{in} ... so V_{out} increases

(b) Cold $V_{out} = 6.0 \times \frac{4.7}{4.7+5.6} = 2.7 \text{ V}$

Hot $V_{out} = 6.0 \times \frac{4.7}{4.7+1.4} = 4.6 \text{ V}$


5 max
check with (a)!

- (c) Replace $4.7 k\Omega$ resistor by a variable resistor
Adjust it to give $V_{out} = 2.5 \text{ V}$ when thermistor is hot.

What value? $2.5 V_{out} = 6.0 \times \left(\frac{R}{R+1.4} \right)$

so $2.5(R+1.4) = 6.0R$

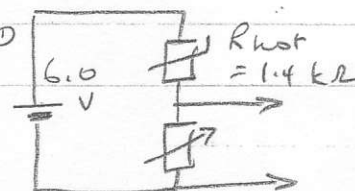$2.5R + 3.5 = 6R$ so $3.5 = 6R - 2.5R = 3.5R$ so $R = 1.0 k\Omega$



- answer to Q4 missing - don't know why - sorry!