

Potentiometer - problems

A Physics
Current Elec.
Potentiometer

1. The Basic circuit

- Can you draw from memory, a potentiometer circuit to measure the emf of a cell.
- Explain how you use the potentiometer, and a test cell of known emf, to measure an unknown cell emf.
- Can you draw the potentiometer circuit, now measuring the terminal p.d. of the test cell under load (driving current through a resistor) - again from memory!!

2 Explain how a potentiometer can measure an emf whereas a meter never can.

3 Here is some data from a potentiometer investigation...

Standard cell emf $E_{st} = 1.25 \text{ V}$

Balance length - standard cell, $l_{st} = 58.3 \text{ cm}$

" - test cell $l_{test} = 82.7 \text{ cm}$

(a) What is the test cell emf?

(b) The test cell is connected to a 10Ω resistor, new balance length $l_{new} = 77.5 \text{ cm}$

Test cell current $I = 120 \text{ mA}$

What is the internal resistance of the test cell?

(c) In another test of the same cell, only this data was recorded.

Resistor = 25Ω , new balance length $l = 79.8 \text{ cm}$

Can you calculate the internal resistance from this data?

4. A potentiometer is modified to measure the tiny emf from a thermocouple. Here is the data...

Driver cell pd = 2.00 V series resistance in driver circuit 96Ω

Resistance of potentiometer wire 4Ω Balance length 26.4 cm .

(a) Draw the full circuit


(b) Calculate the thermocouple emf.

(c) How would you modify the circuit to measure the emf more accurately?

Potentiometer - Answers


A - Physics
Potentiometer

Q1 / 7

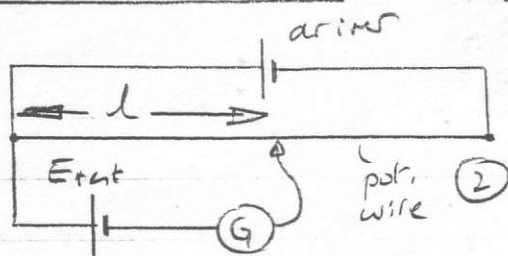

(b) find l_{standard}
balance length for standard cell (3)
Find $l_{\text{test cell}} = \frac{E_{\text{test}}}{E_{\text{standard}}} l_{\text{standard}}$

Q2 / 2

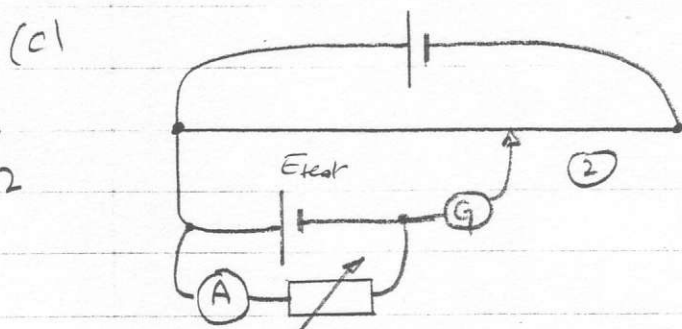

(2) A potentiometer measures a p.d. by balancing it against a known p.d. - so no current flows. So you measure a cell emf without taking current from the cell

(3) (a) $\frac{E_{\text{test}}}{E_{\text{st.}}} = \frac{l_{\text{test}}}{l_{\text{st}}} \Rightarrow E_{\text{test}} = 1.77 \text{ V. (2)}$

(b) how $V_{\text{test cell under load}} = \frac{l_{\text{test}}}{l_{\text{st.}}} \times E_{\text{st.}} = \frac{77.5}{58.3} \times 1.25 = 1.66 \text{ V (1)}$

$E = IR + Ir = V_{\text{ext.}} + Ir \Rightarrow r = (E - V) / I = 0.93 \Omega / 3$

(c) You're not told I - so calculate it using $V = IR$
a bit harder! new test cell p.d. $V_{\text{test}} = 79.8 / 58.3 \times 1.25 = 1.711 \text{ V (1)}$

so cell current $I = V_{\text{test}} / R = 1.711 / 25 = 0.068 \text{ A (1)}$

so from $E = V + Ir \rightarrow r = (E - V) / I = (1.77 - 1.71) / 0.068 = 0.909 (0.91 \Omega) / 3$

Q3 / 8

4. Small emf

Q4 (b) p.d. across wire

$V_{\text{wire}} = \frac{4}{100} \text{ of } 2 \text{ V} = 0.08 \text{ V (2)}$

(or $I = V/R = 2/100 = 0.02 \text{ A}$
 $V_{\text{wire}} = IR_{\text{wire}} = 0.08 \text{ V}$)

so the microamp emf = $26.4 / 100 \times 0.08 = 0.0211 \text{ V / 3}$

(c) Readings are more accurate towards

the right hand end of the wire. You want to reduce p.d. across the wire, or increase p.d. across resistor R - so increase resistor R
(eg if $R = 296 \Omega$ $R_{\text{wire}} = 4/300 \text{ of } 2 \text{ V} = 0.027 \text{ V}$ - just right!)

Q5 / 11.9

