

Electromagnetic Induction

Self-Inductance



A Physics
E11 Induction

A 12V supply is connected to an ammeter, a switch, an inductor (inductance 8 Henries, resistance 4Ω) and a resistor ($R = 20\Omega$), all in series.

The inductor and resistor each have a voltmeter across them. (the voltmeters each have a high but not infinite resistance.)

(a) Draw the circuit. (6)

(b) At the moment the switch is closed....
What is (b) - current ?

(c) - p.d. across coil ?

(d) - p.d. across the resistor? (3)

(e) What are the final steady values of these three quantities? (I , V_{coil} , V_{resistor}) (2+1+2)

(f) The switch is then opened.

What happens to the readings on each of the 3 meters?

(g) Sketch a graph of current against time (put in suitable scales) (3) (4)

(h) Sketch a graph showing how the 2 voltages change with time. (again, suitable scales) (5)

(i) Can you explain why the p.d. across the coil changes as it does when the switch is opened? (No = 0) (3)

(j) Can you sketch a graph to show how current rises from zero to its final value after switching on.

Calculate + show the initial rate of current rise, as well as final current. (5)

(k) Can you sketch a graph to show how the p.d. across the coil changes after switching on? (think back to part (a)!) (4)

E.M. Inductive - Self Inductance

Answers

Phy 11

(a) Circuit

at $t=0$ (b) $I = 0$ A

(c) $V_{\text{coil}} = -12$ V opposing cell

(d) $V_R = 0$ V (no current)

(e) final $I_f = \frac{V}{R_{\text{total}}} = \frac{12}{4+20} = 0.5$ A

(f) $V_{\text{coil}} = I R_{\text{coil}} = 0.5 \times 4 = 2$ V

(g) $V_R = I R_{\text{resistor}} = 0.5 \times 20 = 10$ V (check $V_{\text{coil}} + V_{\text{res.}} = 12$ V)

(f) open switch... ammeter - reading drops instantly to 0

$V_{\text{coil}} = V_L$ jumps up briefly to large p.d. (induced back emf)

V_R - drops instantly to 0

(g) current / time

(h) two p.d.s / time

(i) Explain...

current and, therefore magnetic flux change v. rapidly... so this induces a large reverse emf across coil... that slowly discharges through the voltmeter

(j) Switching on...





initially... at $t=0$

$$E = 12 \text{ V} = L \frac{dI}{dt}$$

$$\text{so } \frac{dI}{dt} = \frac{12}{L} = \frac{12}{8} = 1.5 \text{ A/sec}$$

$$I_{\text{final}} = \frac{V}{R_{\text{total}}} = \frac{12}{24} = 0.5 \text{ A (see (e))}$$

(k) And finally...

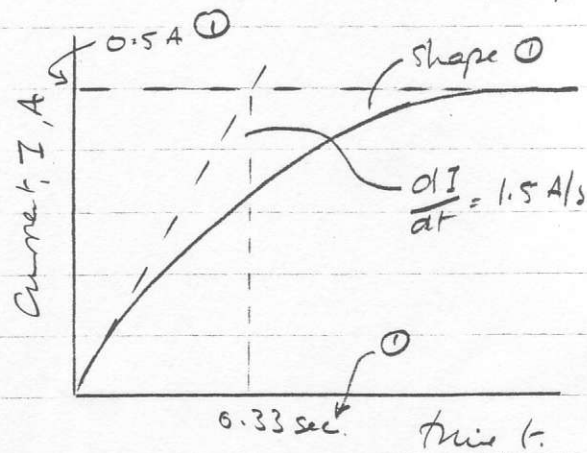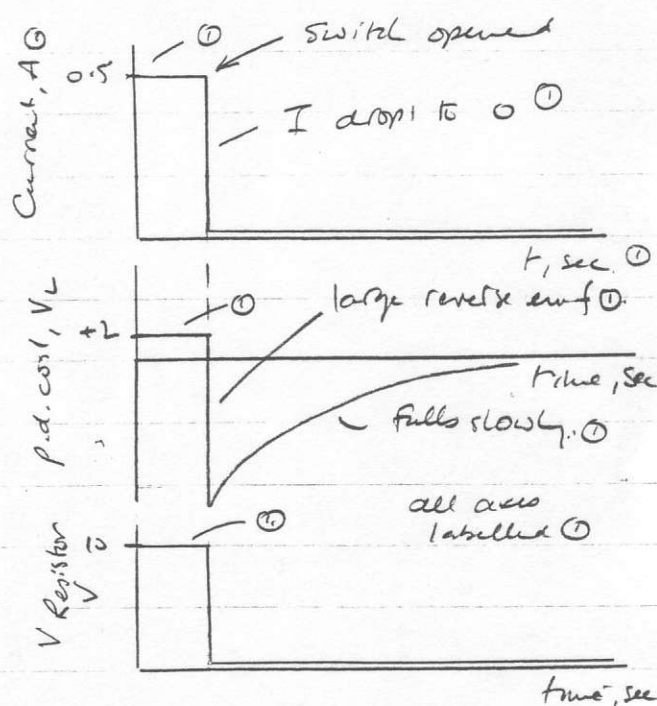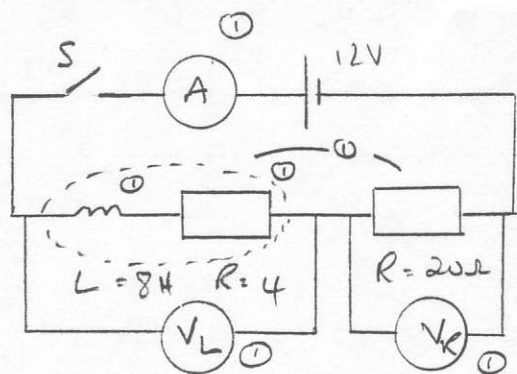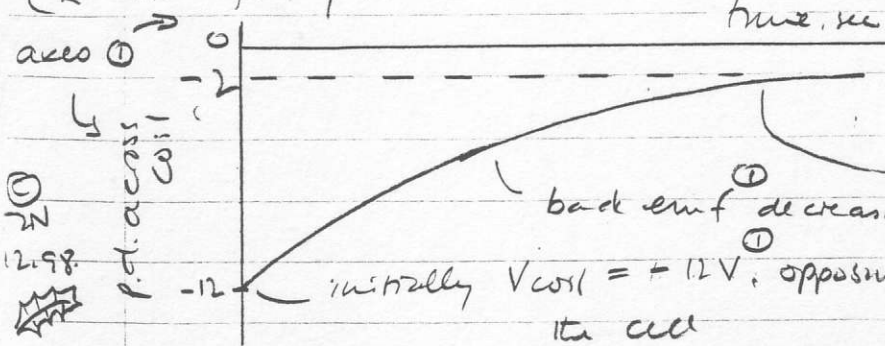

V_{coil} finally = -2 V with steady 0.5 A current