

1.2. A current of $60 \mu\text{A}$ flows for 12 ms , driven by a p.d. of 25 V .

- How much charge has flowed? (2)
- How many electrons is this? (2)
- How much energy has been produced as heat? (2)
- What power is produced while the current flows? (2)


2. a) Is a filament bulb an Ohmic or a non-ohmic device? Explain your answer. (3)

Sketch V/I graphs for

- an ldr in the light and dark states (3)
- a diode (3)


3. How does a solution of copper sulphate conduct current, compared to a metal? (4)

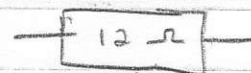4. A 240 V mains shower has a 12 Ohm heating element in it.



- What is the power of the shower? (2)
- What resistance would you need for a power of 3 kW ? (2)
- The 12 Ohm element is made of resistance wire of 0.5 mm diameter. How long is the wire? (4)
- What is the drift velocity of electrons in this wire when it is connected to 240 V ? The metal has 5×10^{28} free electrons/ m^3 (4)

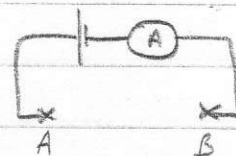5. a) A student connected a metal wire between A and B, and noted the current reading. She then heated the wire in a Bunsen flame. State and explain the change in current reading. (3)



- The student replaced the metal wire with a thermistor. State and explain the change in current on heating the thermistor. (3)

AS - Unit 1 - Half Unit Test 2/02

6. a) A Science Teacher puts a new 1.5 V cell in his mini disc player, circuit resistance 20Ω . He plays his favourite garage and trance music for 2 hours, during which time the external cell p.d. drops steadily to 1.2 V . Sketch a graph to show how the current varies in this time, and calculate the total charge passed. (6)
- b) The teacher puts in a new type of cell, with an emf of 1.6 V and internal resistance 0.8Ω . What is the terminal p.d. of this cell when it runs the mini disc player? (3)
- c) How much thermal energy is dissipated in the cell in the first 5 minutes? (assume the internal resistance stays constant. (3)

Q. no. 1. 2. 3. 4. 5. 6. Total

 1/8 1/9 1/4 1/12 1/6 1/12 51


AS Physics - Unit - Unit 2 Test

Answers



1. (a) $Q = It = 60 \times 10^{-6} \times 12 \times 10^{-3} = 7.2 \times 10^{-7} \text{ C}$ (b) $Q = \frac{7.2 \times 10^{-7}}{1.6 \times 10^{-19}} = 4.5 \times 10^{12} \text{ electrons}$
 (c) $E = QV = ItV = 7.2 \times 10^{-7} \times 25 = 1.8 \times 10^{-5} \text{ J}$
 (d) $P = IV = 60 \times 10^{-6} \times 25 = 1.5 \times 10^{-3} \text{ Watts}$

1/8

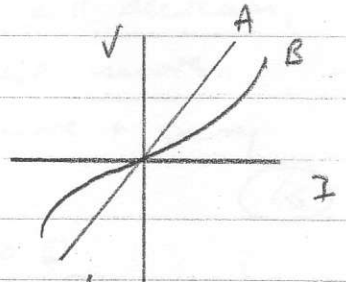2. (a) An ohmic device has a constant R , so the V/I graph is linear. A bulb does not have a constant R because its temperature changes - so it's non-ohmic





b) $I \propto V$ - dark axis (c) diode

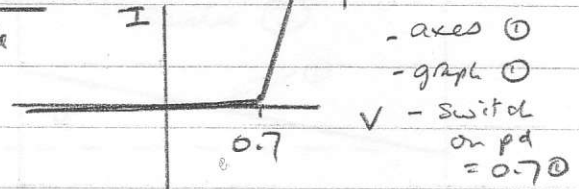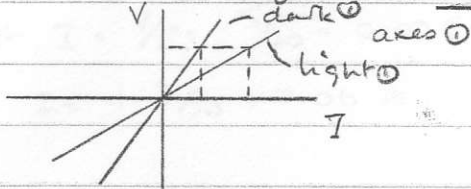

- axes
 - graph
 - switch on pd = 0.7V

1/9

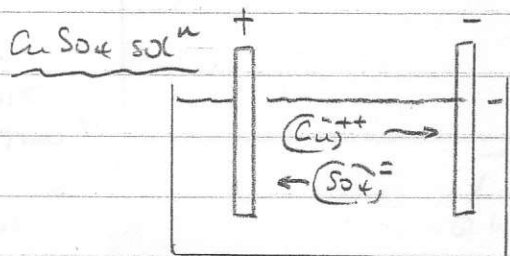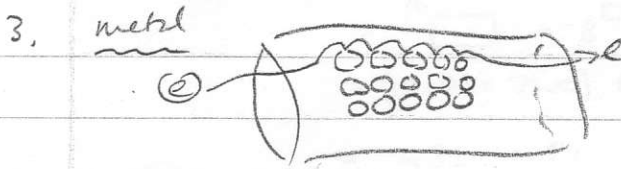

each atom releases 1 "free" electron.

... electrons drift from atom to atom ... slowed down by atomic collisions.

+ and - charged ions move through solution to the oppositely charged electrode

1/4

4. a) $P = IV = \frac{V^2}{R} = \frac{240^2}{12} = 4800 \text{ W}$ (or $I = \frac{V}{R} = 20 \text{ A} \dots P = IV = 4800 \text{ W}$)

b) for 3 kW power... $R = \frac{V^2}{P} = \frac{240^2}{3000} = 19.2 \Omega$

(or $I = P/V = 3000/240 = 12.5 \text{ A} \dots R = V/I = 240/12.5 = 19.2 \Omega$)

c) Use $R = \frac{\rho l}{A}$ Area $A = \pi r^2 = \pi \times (0.25 \times 10^{-3})^2 = 1.96 \times 10^{-7} \text{ m}^2$

so $l = RA/\rho = \frac{12 \times 1.96 \times 10^{-7}}{1.2 \times 10^{-6}} = 1.96 \text{ m}$

d) drift velocity... $I = nAve \Rightarrow v = I/nAe$

see part (a) $= \frac{20}{5 \times 10^{28} \times 1.96 \times 10^{-7} \times 1.6 \times 10^{-19}} = 0.013 \text{ m/s}$

or $1.3 \times 10^{-2} \text{ m/s}$

1/12

Unit 1 Test - $\frac{1}{2}$ Unit Test Answers $\frac{2}{10/2}$

5. (a) The Current reading will decrease ^①, because the resistance will increase ^① because the metal atoms are vibrating more violently ^①

(b) The current will increase ^①, because Resistance will decrease ^①, because the extra thermal energy has freed more electrons ^① from their atoms to be able to move + carry current

6. a) start $I = V/R = 1.5/20 = 0.075 \text{ A}$

and $I = 1.2/20 = 0.06 \text{ A}$


Charge passed = area under graph ^①.

= A  + B 

= $(0.06 \times 7200) + \frac{1}{2} (0.015 \times 7200)$

= $432 + 54$

= 486 Coulombs ^①

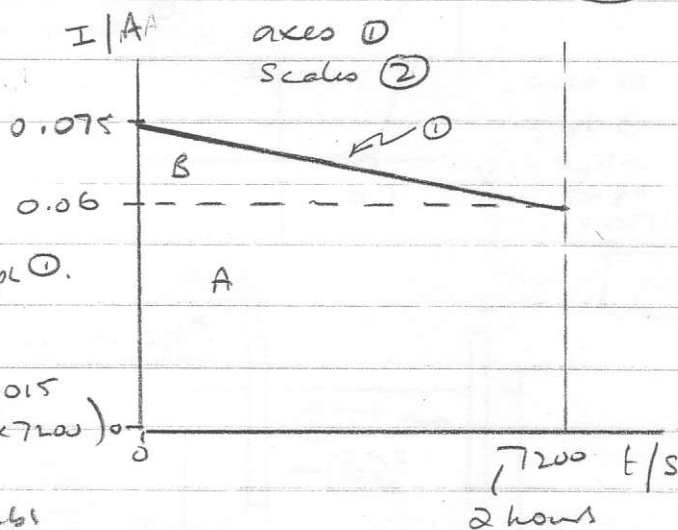

b) A "real" cell ... $E = IR + Ir$ ^①

$1.6 = I(20 + 0.8)$


so $I = 0.0769 \text{ A}$ ^①

So "lost" p.d. inside cell = $Ir = 0.0769 \times 0.8$

= 0.0615 V

So new cell terminal p.d. = $1.6 - 0.0615$

= 1.54 V ^①

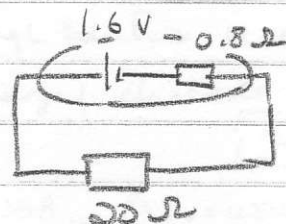

c) Internal heat produced = power $\times$ t

= $IV \times t$ ^①

= $0.0769 \times 0.0615 \times 300$ ^①

= 1.42 Joules ^①

p.d. across r_{internal}

secs in 5 min