


Thermistors and Resistance

AS Phys. 2.1

The current flowing through a thermistor at different temperatures is measured with this circuit →

The results are: —

Temp, °C	0	10	25	40	54	76	100
Current, mA	7.4	9.0	11.9	15.6	20.2	28.8	41.7

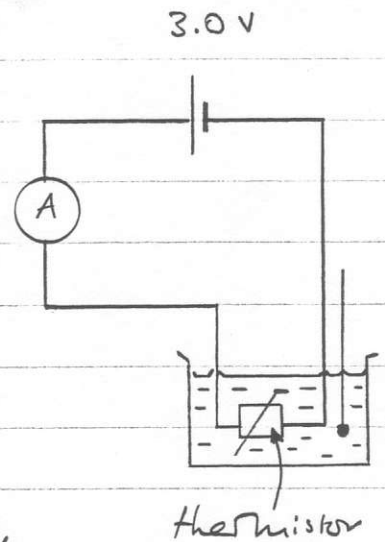

- Calculate the resistance at each temperature. Put all values of temperature, current and resistance in a table. Plot a graph of resistance against temperature over the range 0 – 100 °C (table: 6, graph: 7)
- Why does the resistance of the thermistor decrease as its temperature rises? (3)
- You want to use the circuit to measure temperature over the range 20 – 80 °C to an accuracy of $\pm 1^\circ\text{C}$. You have 4 different types of meters, with ranges....
0 – 10 mA, 0 – 50 mA, 0 – 100 mA, and 0 – 500 mA.
Which one should you use, and why? (2)
- What is the change in current for a 1°C change in temperature at 20 °C? 80 °C? (4)
- Sketch a suitable scale for the current meter in (c) that will enable you to measure temperature to the required accuracy.
- Where on the temperature range 20 – 80 °C is your electronic thermometer most accurate? Explain your answer. (3)
- You want to use the circuit in a thermostat to control the temperature of water at $37 \pm 2^\circ\text{C}$. What are the maximum and minimum currents for this range? (2)
- The current flowing through the thermistor generates heat. What heating power is produced at 60 °C? (4)
- Can you suggest how the system in the diagram can be used to measure the temperature of water in a car engine? If the normal temperature is 90 °C what would the current be? (4)

(a)


$T, ^\circ\text{C}$	0	10	25	40	54	76	100
I, mA	7.4	9.0	11.9	15.6	20.6	28.8	41.7
R, Ω	405	333	252	192	149	104	71.9

all answers ②
3 s.f. accuracy ①

⑥

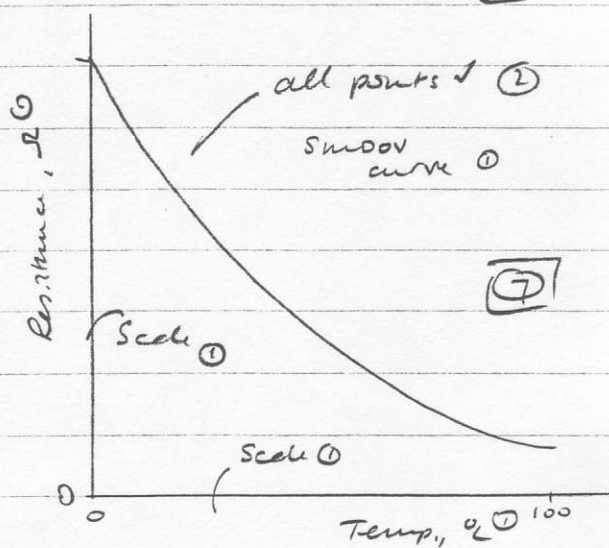(b) Why $R \downarrow$ as $T \uparrow$

- as Temp. increases the atoms have more thermal energy ①
(vibrate more $\frac{1}{2}$).... this releases some electrons from their atoms ①.... so there are more electrons free to carry charge ①



⑦

c) the best meter

at 20°C $R = 280 \Omega$ $I_{20} = \frac{V}{R} = 0.0107 \text{ A} = 10.7 \text{ mA}$ ①

at 80°C $R = 96 \Omega$ $I_{80} = 0.0312 \text{ A} = 31.2 \text{ mA}$ ①


So the max. current is 31 mA... best meter is the 0-50 mA one ①

d) $R_{at 21} = 272 \Omega$, $I_{21} = 0.011 \text{ A} = 11.0 \text{ mA}$ ①

$R_{at 81} = 94 \Omega$, $I_{81} = 0.0319 \text{ A} = 31.9 \text{ mA}$ ①

So change in I for 1°C Temp change

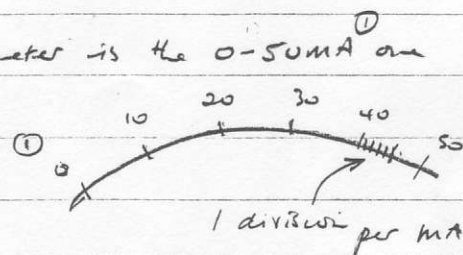at 20° is $11.0 - 10.7 = 0.3 \text{ mA}$ ① at 80°C is $31.9 - 31.2 = 0.7 \text{ mA}$ ①



e) See sketch. any scale ① shows 10s of mA ① shows 1 mA divisions ①

f) The Thermometer is most accurate at high Temp. (around 80°C) because at that end a 1°C change gives the biggest current change ①

g) Thermistor.... $T = \dots 37 - 2 = 35^\circ\text{C}$ $R = 208$ $I = 0.0144 \text{ A} = 14.4 \text{ mA}$ ①

$37 + 2 = 39^\circ\text{C}$ $R = 194$ $I = 0.0155 \text{ A} = 15.5 \text{ mA}$ ①

h) heat production.... Heating power $P = IV = I^2R = \frac{V^2}{R}$ ① ← the most useful.

at 60°C $R = 136 \Omega$ so Power $P = \frac{3^2}{136} = 0.066 \text{ Watts}$ ①

i) Car engine.... put thermistor in

the engine's water system....

Mark the ammeter scale

as cold... hot ①

at 90°C $R = 84 \Omega$ for 3V $I = 36 \text{ mA}$

So for $4 \times 3 = 12 \text{ V}$ $I = 4 \times 36 = 144 \text{ mA}$ ①

